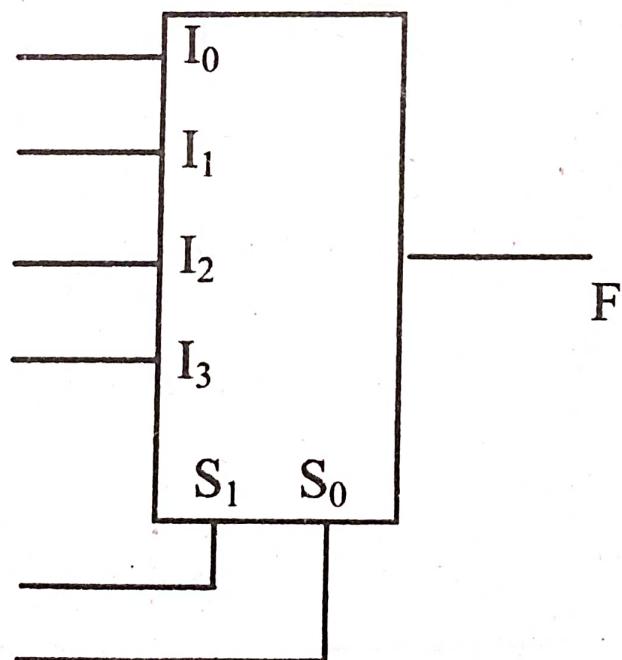



22. The Boolean equation $F(X, Y, Z) = \pi(2, 4, 7)$ is to be implemented using 4×1 multiplexer shown in figure. Which one of the following choices of inputs to multiplexer will realize the Boolean function?



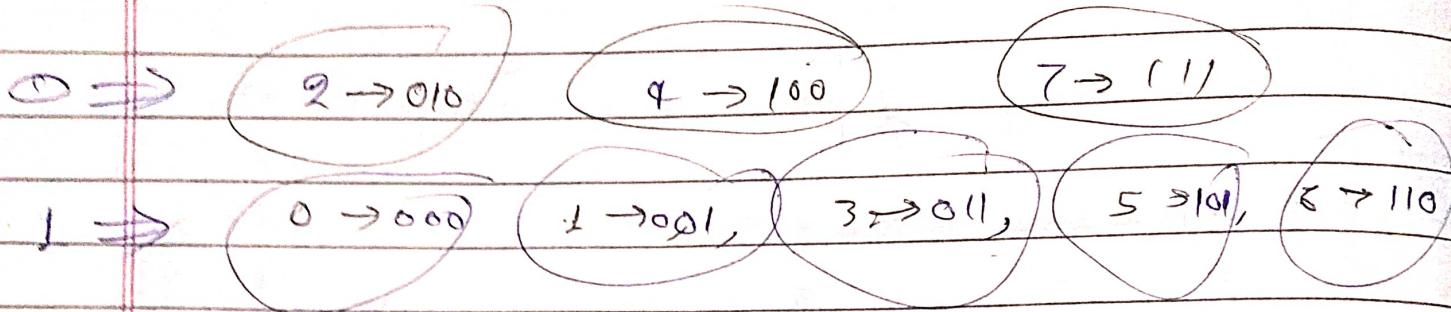- (a) $(I_0, I_1, I_2, I_3, S_1, S_0) = (\bar{X}, 1, X, \bar{X}, Y, Z)$
- (b) $(I_0, I_1, I_2, I_4, S_1, S_0) = (0, 1, \bar{X}, X, Y, Z)$
- (c) $(I_0, I_1, I_2, I_4, S_1, S_0) = (1, 0, \bar{X}, X, \bar{Y}, Z)$
- (d) $(I_0, I_1, I_2, I_3, S_1, S_0) = (1, 0, X, \bar{X}, Y, \bar{Z})$

$$F = \pi M(2, 4, 7) = \Sigma m(0, 1, 3, 5, 6)$$

$$F = I_0 \bar{s}_1 \bar{s}_0 + I_1 \bar{s}_1 s_0 + I_2 s_1 \bar{s}_0 + I_3 s_1 s_0$$



$$I_0 \bar{s}_1 \bar{s}_0 = \begin{array}{c|cc} x & y & z \\ \hline 0 & 0 & 0 \\ 1 & 1 & 1 \\ 0 & 0 & 0 \\ 1 & 1 & 0 \end{array} \xrightarrow{\pi} \begin{array}{c} x \\ \bar{x} \\ \bar{x} \\ x \end{array}$$

$$I_1 \bar{s}_1 s_0 = \begin{array}{c|cc} x & y & z \\ \hline 0 & 0 & 1 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{array} \xrightarrow{\pi} \begin{array}{c} x \\ x \\ F \end{array}$$

$$I_2 s_1 \bar{s}_0 = \begin{array}{c|cc} x & y & z \\ \hline 0 & 1 & 0 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{array} \xrightarrow{\pi} \begin{array}{c} x \\ \bar{x} \\ x \end{array}$$


$$I_3 s_1 s_0 = \begin{array}{c|cc} x & y & z \\ \hline 0 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 0 \end{array} \xrightarrow{\pi} \begin{array}{c} x \\ x \\ x \\ x \\ y \\ z \end{array}$$

(a) $\boxed{(I_0, I_1, I_2, I_3, s_1, s_0)}$

$$= (\bar{x}, \perp, x, \bar{x}, y, z)$$

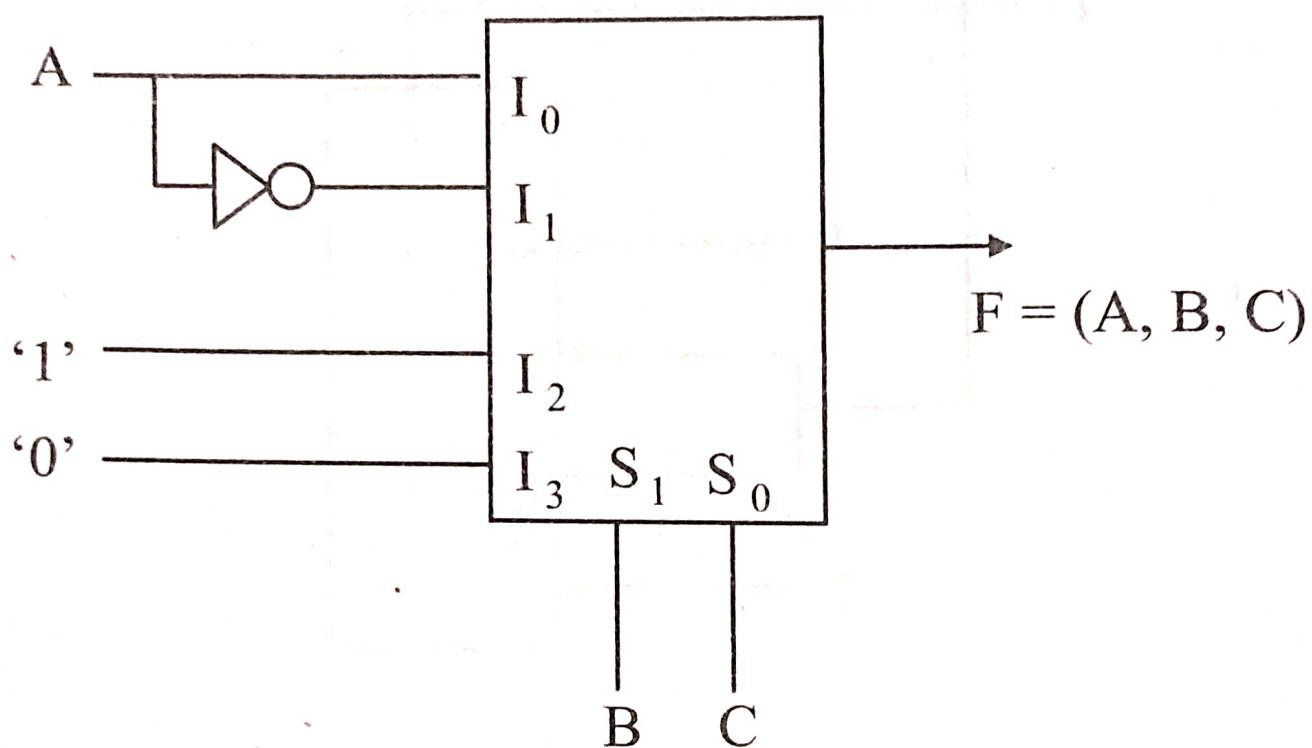23. A 4×1 MUX is used to implement a 3- input Boolean function as shown in figure.

The Boolean function $F(A, B, C)$ implemented is



- (a) $F(A, B, C) = \sum m(1, 2, 4, 6)$
- (b) $F(A, B, C) = \sum m(1, 2, 6)$
- (c) $F(A, B, C) = \sum m(2, 4, 5, 6)$
- (d) $F(A, B, C) = \sum m(1, 5, 6)$

(a) 233

$$F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{L} \cdot B\overline{C} + \overline{a} \cdot B\overline{C}$$
$$\cancel{\overline{B}(A \oplus C)} + \overline{B}\overline{C}$$


$$F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + \overline{a}\overline{B}\overline{C}$$

↓ ↓ ↓ ↓
4 1 6 2

(a)

$$F = \sum m(1, 2, 4-6)$$

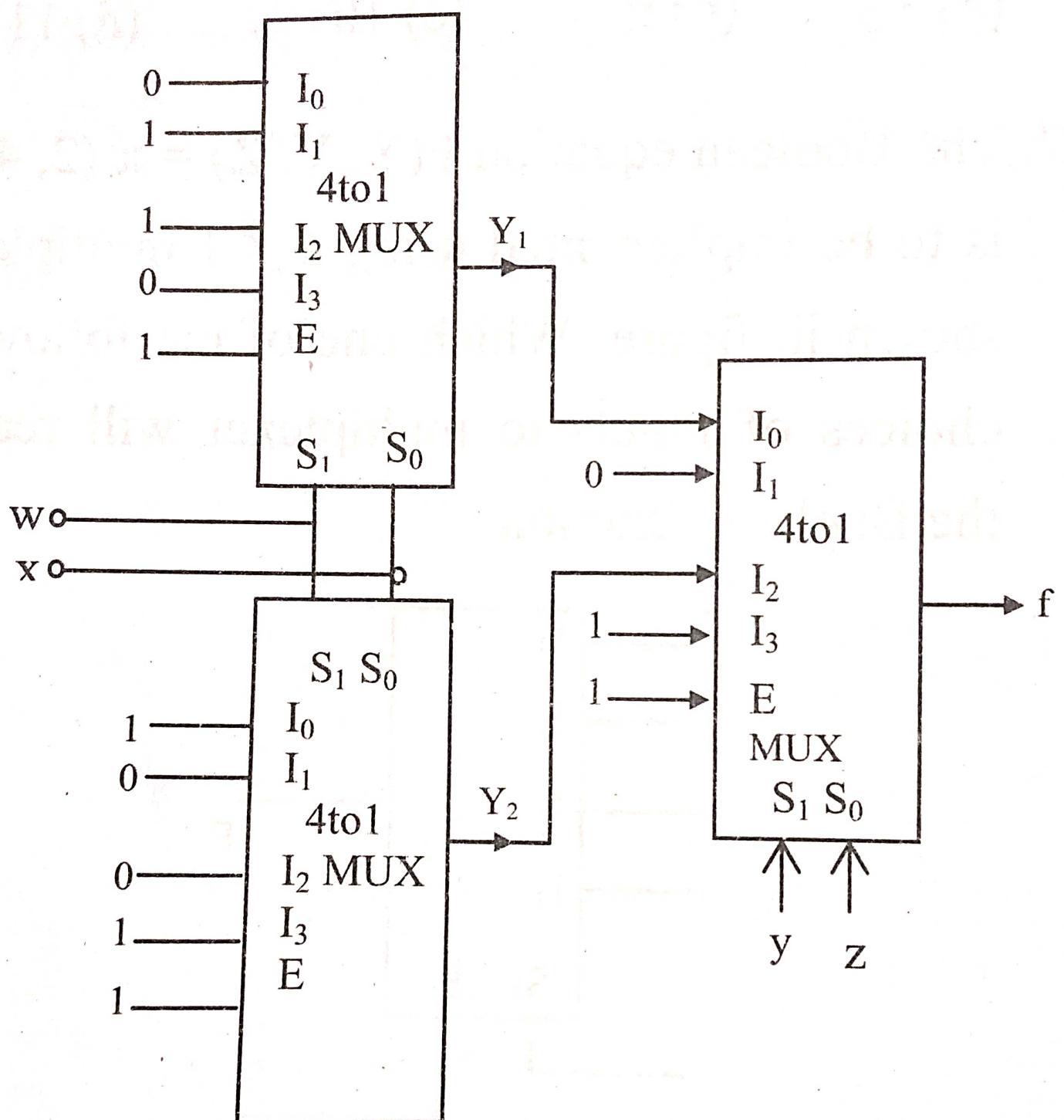24. The function realized by the given multiplexer circuit is



- (a) $f(w, x, y, z) = \sum m(2, 3, 4, 7, 8, 11, 14, 15)$
 $+ d(1, 10, 12)$
- (b) $f(w, x, y, z) = \sum m(2, 3, 4, 7, 8, 11, 14, 15)$
- (c) $f(w, x, y, z) = \pi M(2, 3, 4, 7, 8, 11, 14, 15)$
 $.d(1, 10, 12)$
- (d) $f(w, x, y, z) = \pi M(2, 3, 4, 7, 8, 11, 14, 15)$

(b) 24 P

$$Y_1 = E(0 \cdot \bar{w}\bar{x} + 1 \cdot \bar{w}x + 1 \cdot w\bar{x} + 0 \cdot wx)$$

$$Y_1 = \textcircled{5} \cdot (w \oplus x)$$

10

$$Y_2 = 1 \cdot (\bar{w}\bar{x} + 0 \cdot \bar{w}x + 0 \cdot w\bar{x} + 1 \cdot wx)$$

$$Y_2 = (w \oplus x)$$

10

$$F = 1 \cdot (Y_1 \cdot \bar{y}\bar{z} + 0 \cdot \bar{y}z + Y_2 \cdot y\bar{z} + 1 \cdot yz)$$

$$F = [(\bar{w}x + w\bar{x})\bar{y}\bar{z} + (\bar{w}\bar{x} + wx)\bar{y}z + (\bar{w} + w)(x + \bar{x})yz]$$

$$F = \bar{w}x\bar{y}\bar{z} + w\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}y\bar{z} + wx\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}\bar{x}y\bar{z} + w\bar{x}yz$$

$$\begin{matrix} & \uparrow \\ & 4 & 8 & 12 & 14 & 7 & 3 & 11 \\ \checkmark & \checkmark \\ & \uparrow & & \uparrow & & \uparrow & & \uparrow \\ & 9 & & 10 & & 13 & & 15 \end{matrix}$$

b

$$F = \sum m (2, 3, 4, 7, 8, 11, 14, 15)$$

25. Minimum size of ROM required to implement following set of Boolean equations is

$$F_1(w,x,y,z) = \sum m(0,1,2,5,7,12,13,15)$$

$$F_2(w,x,y,z) = \sum m(0,5,6,9,13,15)$$

$$F_3(w,x,y,z) = \sum m(6,7,9,12,14,15)$$

(a) 16×4

(b) 16×3

(c) 16×8

(d) 16×12

(b) Q51

$$F_1(w, n, y, z) = \Sigma m(0, 1, 2, 5, 7, 12, 13, 15)$$

$$F_2(w, n, y, z) = \Sigma m(0, 5, 6, 9, 13, 15)$$

$$F_3(w, n, y, z) = \Sigma m(6, 7, 9, 12, 14, 15)$$

Solⁿ

We have 9 variable of f^n :

$$\text{minterm} = 16$$

Decoder size = 4×16


3 function required implement

3 lines needed

[ROM Size = 16×3]

(b) (16×3)

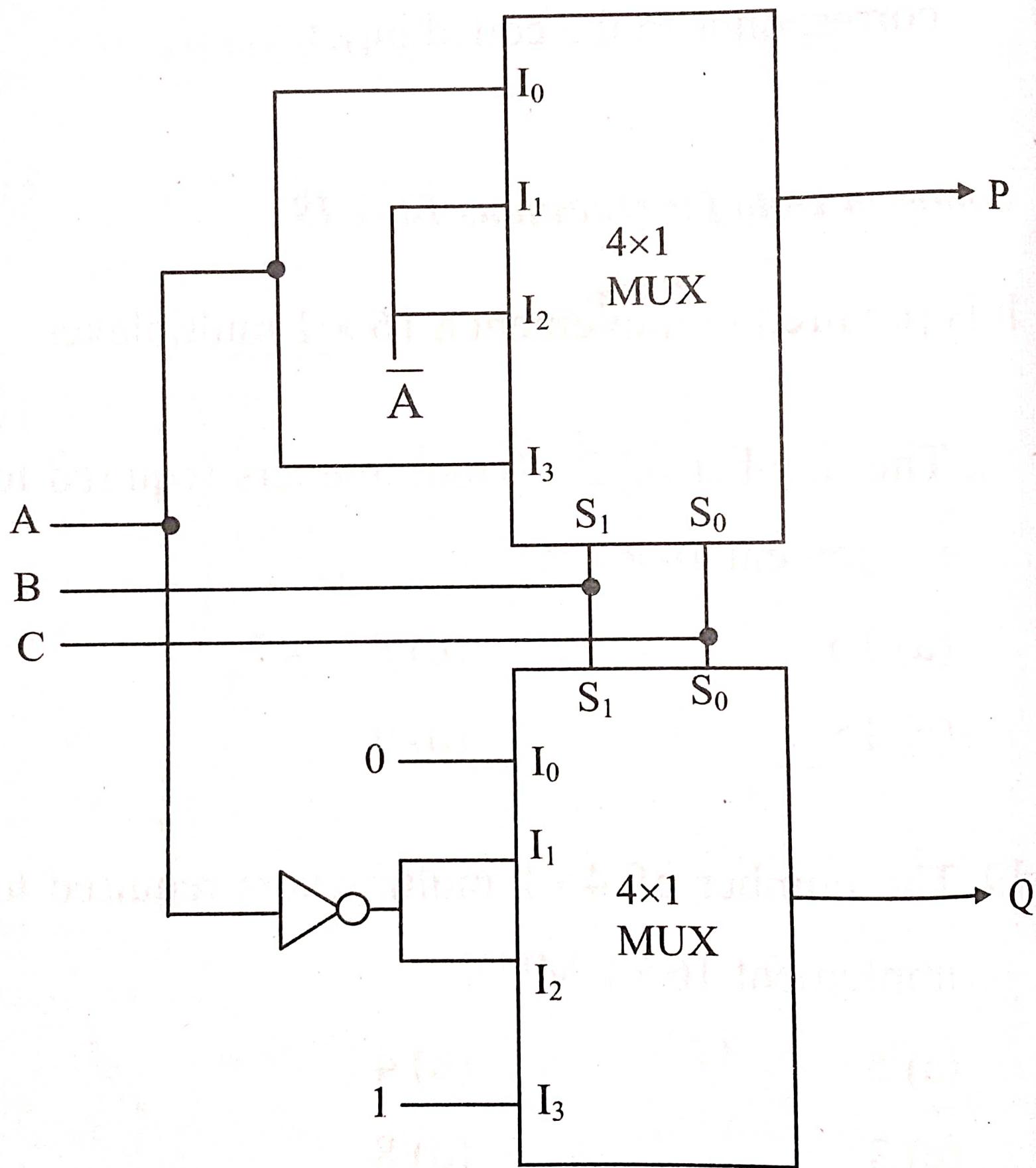26. Identify the output equations for the following circuit.



$$(a) P(A,B,C) = \Sigma m (1, 2, 4, 7)$$

$$Q(A,B,C) = \Sigma m (2, 3, 4, 7)$$

$$(b) P(A,B,C) = \Sigma m (1, 2, 4, 7)$$

$$Q(A,B,C) = \Sigma m (1, 2, 3, 7)$$

$$(c) P (A,B,C) = \Sigma m (1, 2, 4, 7)$$

$$Q(A,B,C) = \Sigma m (3, 5, 6, 7)$$

$$(d) P(A,B,C) = \Sigma m (3, 5, 6, 7)$$

$$Q(A,B,C) = \Sigma m (1, 2, 4, 7)$$

(b) Q6 $P = \overline{ABC} + \overline{A}\overline{B}C + \overline{AB}\overline{C} + A\overline{B}C$

$\boxed{P = \sum m(1, 2, 4, 7)}$

$$\Phi = 0 \cdot \overline{BC} + \overline{A}\overline{B}C + \overline{AB}\overline{C} + 1 \cdot BC$$


$$\Phi = \overline{A}\overline{B}C + \overline{AB}\overline{C} + \overline{ABC} + ABC$$

$C_1 \quad C_2 \quad C_3 \quad C_7$

$\boxed{\Phi = \sum m(1, 2, 3, 7)}$

(b)

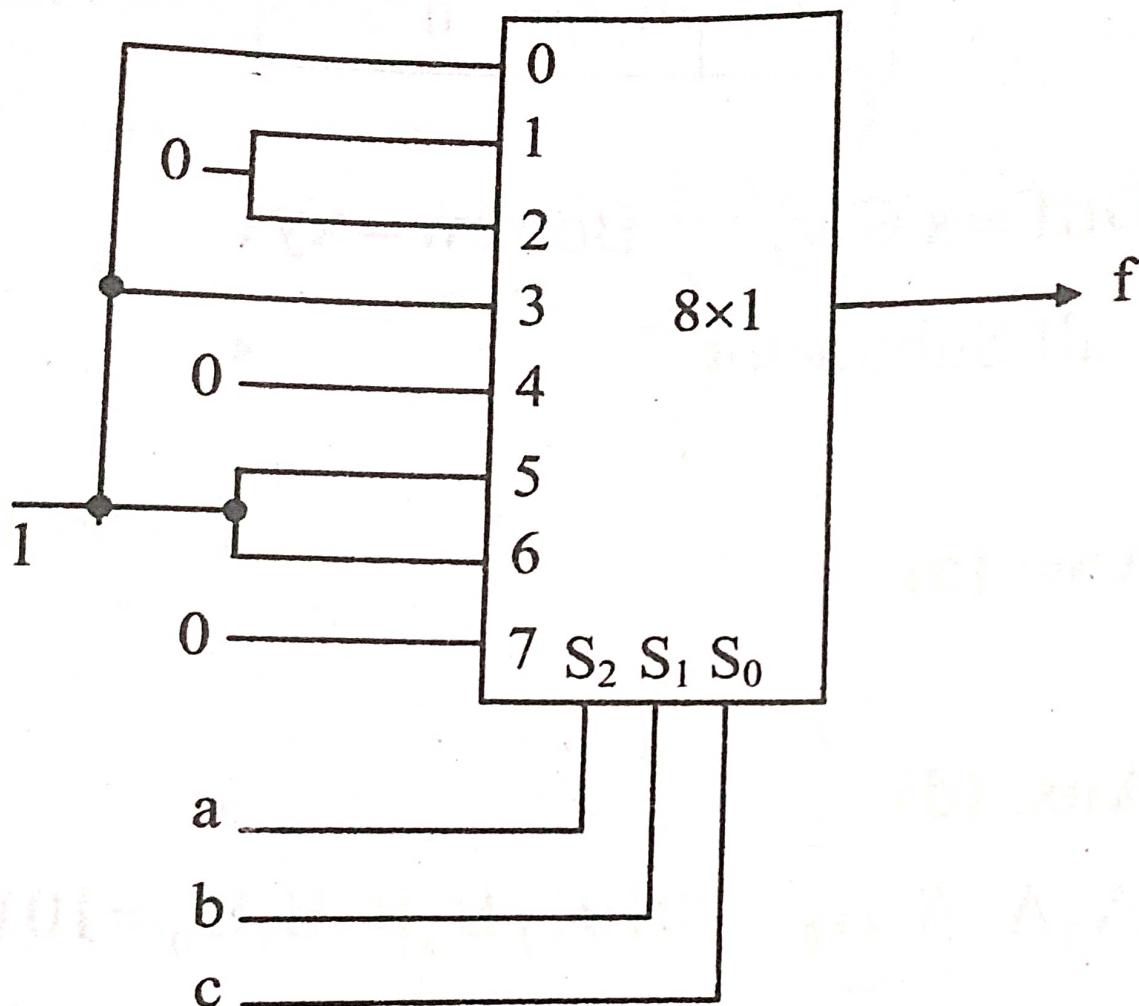27. The Boolean equation representing the following circuit is



- (a) $f(a, b, c) = \sum m(1, 2, 4, 7)$
- (b) $f(a, b, c) = \sum m(3, 5, 6, 7)$
- (c) $f(a, b, c) = \sum m(0, 3, 5, 6)$
- (d) $f(a, b, c) = \sum m(1, 2, 5, 7)$

(c) 27) $F = 1 \cdot \bar{a} \bar{b} \bar{c} + 0 \cdot \bar{a} \bar{b} c + 0 \cdot \bar{a} b \bar{c} + 1 \cdot \bar{a} b c + 0 \cdot a \bar{b} \bar{c} + 1 \cdot a \bar{b} c + 1 \cdot a b \bar{c} + 0 \cdot a b c$

$$F = \bar{a} \bar{b} \bar{c} + \bar{a} b c + a \bar{b} c + a b \bar{c}$$

$\complement_0 \quad \complement_3 \quad \complement_5 \quad \complement_6$

(c) $F = \text{sum } (0, 3; 5, 6)$

28. To design a 2-bit comparator the following are needed
- (a) Two 1-bit comparators, 2 AND gates, 1 OR gate
 - (b) Two 1-bit comparators, 3 AND gates, 2 OR gates
 - (c) Three 1 bit comparators, 2 AND gates, 1 OR gate
 - (d) Three 1-bit comparators, 3 AND gates, 2 OR gates

b) 28) Design 2-bit comparator


Solⁿ

$$\bar{G} = G_1 + E_1 \cdot G_0$$

$$A = A_1 A_0, \quad B = B_1 B_0 \Rightarrow A > B$$

$$(E = E_1 \cdot E_0) \Rightarrow \# = B$$

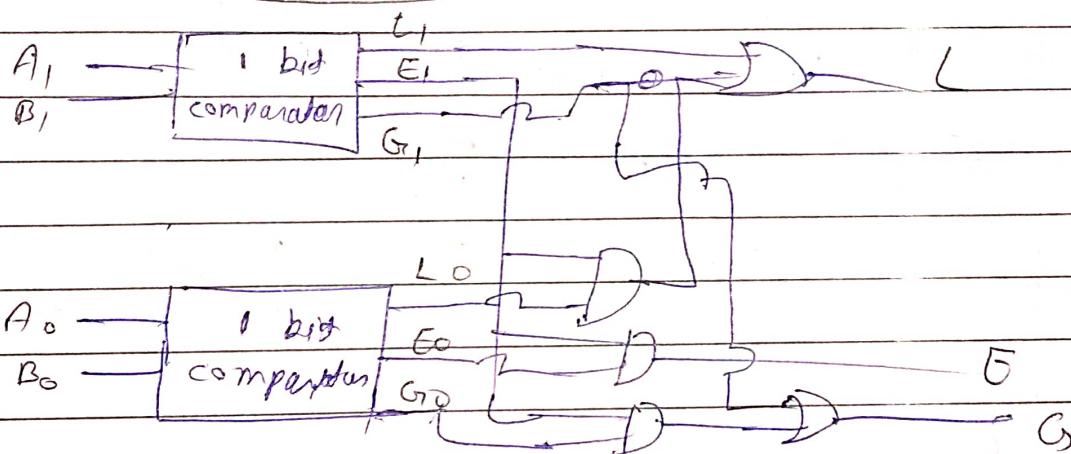
$$(L = L_1 + E_1 \cdot L_0) \Rightarrow \# \Rightarrow A < B$$



b) Two - 1-bit comparators 3-ANP, 2-OR

29. What are basic gates required to implement a full adder?

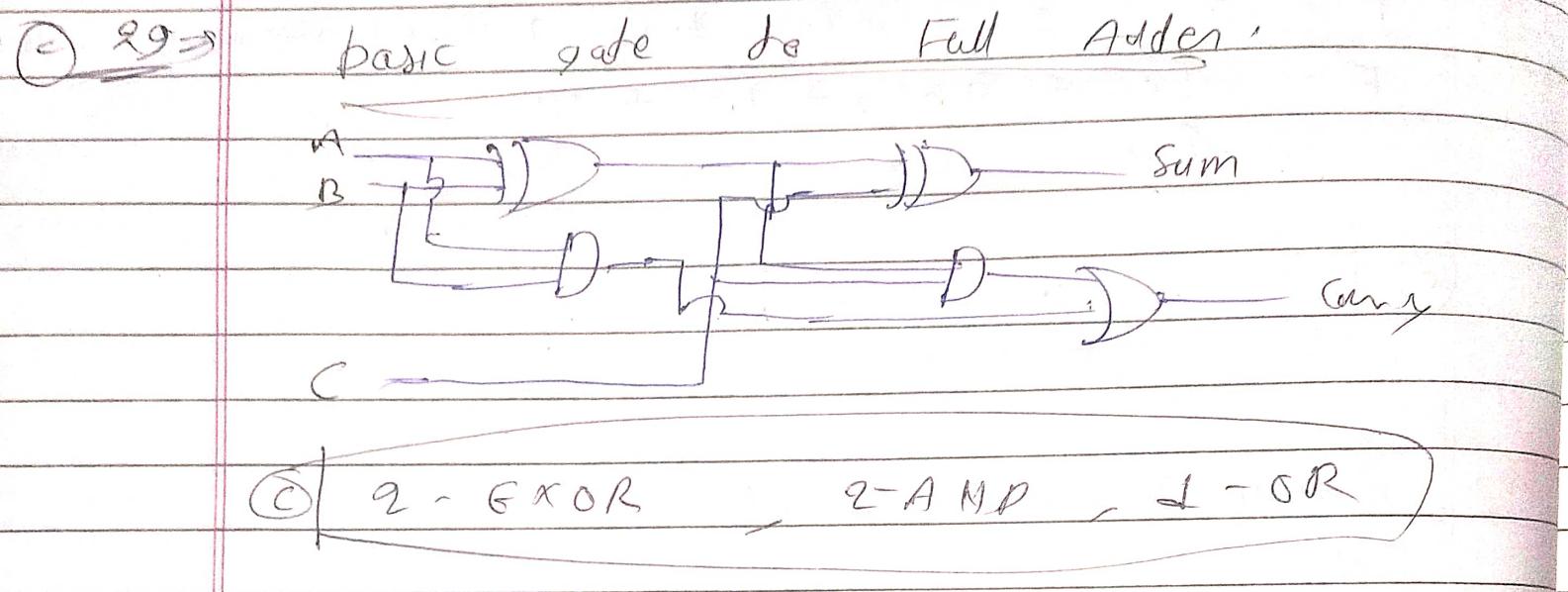- (a) 1-EX-OR gate, 1 AND gate
- (b) 2-EX-OR gates, 1 OR gate
- (c) 2EX-OR gates, 2 AND gates, 1 OR gate
- (d) 1EX-OR gates, 2 AND gates, 2 OR gates



30. How many half adders are required to implement the following expressions.

$$D = \overline{A}BC + A\overline{B}C, E = A \oplus B \oplus C$$


$$F = \overline{A}C + ABC + \overline{B}C$$

- | | |
|-------|-------|
| (a) 2 | (b) 3 |
| (c) 4 | (d) 1 |

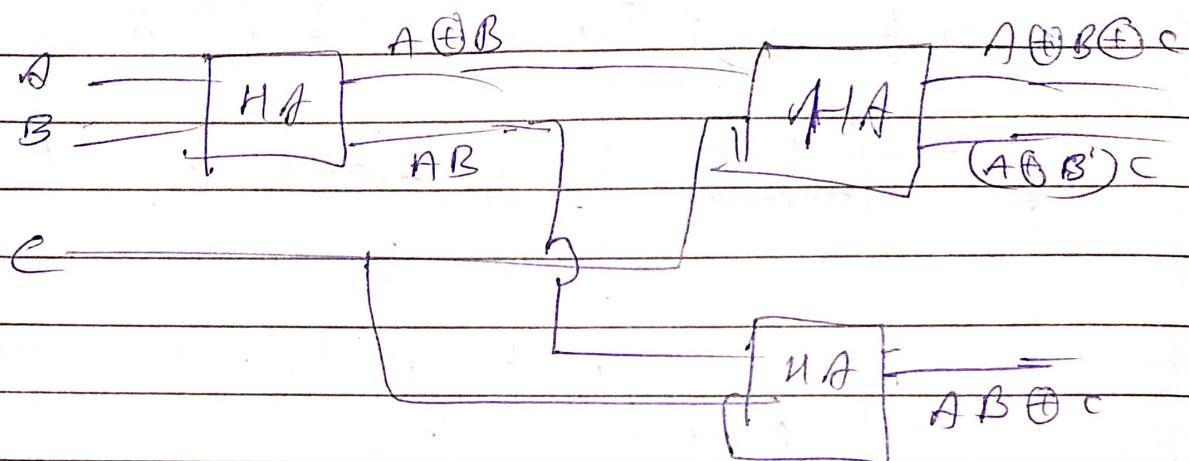(b) $\xrightarrow{30}$

$$D = C(A \oplus B) \quad E = A \oplus B \oplus C$$

$$F = \overline{AB}c + AB\bar{C} = AB \oplus C$$



(b) $3 - HA$

31. While designing BCD(ABCD) to 9's complement BCD(PQRS), what is the expression for 'Q'?

- (a) $B \oplus \overline{C}$
- (b) BC
- (c) $B \oplus C$
- (d) $\overline{B} \oplus C$

(C) 317

BCP

A	B	C	D	(q's of BCP)s	Des.
0	0	0	0	1 0 0 1	0 0
0	0	0	1	1 0 0 0	1 0
0	0	1	0	0 1 1 1	2 1
0	0	1	1	0 1 1 0	3 1
0	1	0	0	0 1 0 1	4 1
0	1	0	1	0 1 0 0	5 1
0	1	1	0	0 0 1 1	6 0
0	1	1	1	0 0 1 0	7 0
1	0	0	0	0 0 0 1	8 0
1	0	0	1	0 0 0 0	9 1
<hr/>				0/1	
<hr/>				10 X	
<hr/>				11 X	
<hr/>				12 1 X	
<hr/>				13 X	
<hr/>				K 15 X	
<hr/>				Q	

$$\Phi = \sum m(2, 3, 4, 5) + \sum d(10, 11, 12, 13, 14, 15)$$

Post
cane

$\bar{A}B$	$\bar{C}D$	$\bar{C}\bar{D}$	CD	$\bar{C}\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1	1	1	1
AB	X=1	X=1	X=0	X=0
$A\bar{B}$			X=1	X=1

(C) $\Phi = B \oplus C$

Teacher's Signature


32. What are the components required to realize
 $10 \times 1k$ decoder?

- (a) '4' 8×256 decoders & '1' 2×4 decoder
- (b) '8' 8×256 decoders & '2' 2×4 decoders
- (c) '4' 8×256 decoders & '2' 2×4 decoders
- (d) '8' 8×256 decoders & '1' 2×4 decoder.

① 32 →

component required


10×1024 decoder

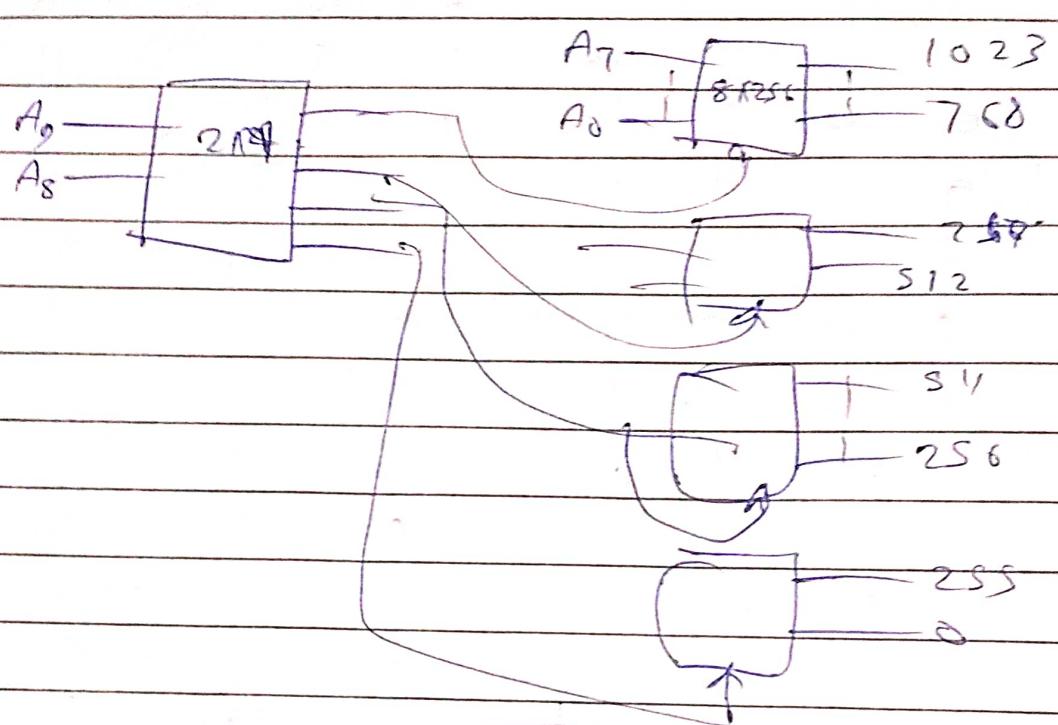

②

$q \Rightarrow 8 \times 256 \Rightarrow 1 \rightarrow 2 \times 4$

33.

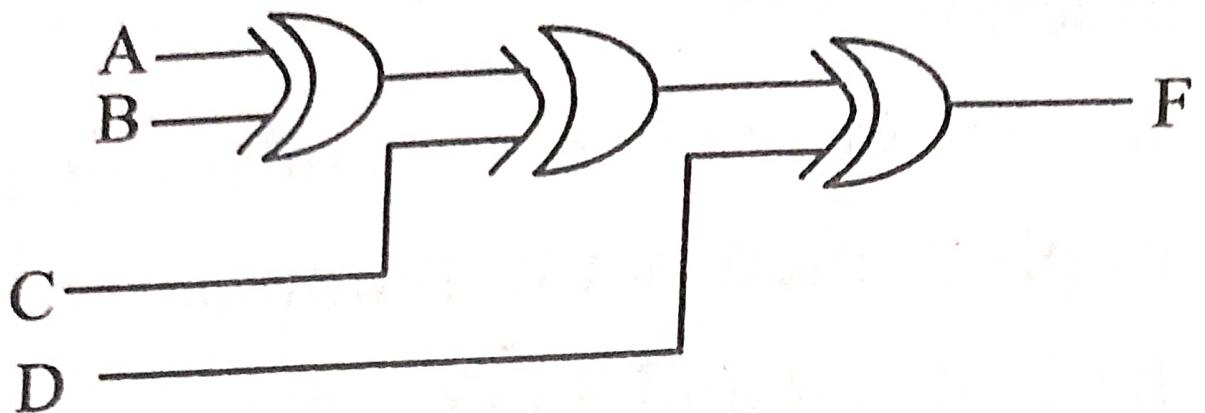

The above circuit is a

- (a) Even parity generator
- (b) Odd parity generator
- (c) Even parity checker
- (d) Odd parity checker

~~a) 33~~) $F = ((A \oplus B) \oplus C) \oplus D$

(a) Even parity generator