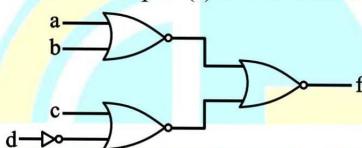


Digital Electronics

1. Logic Gate

Q.1 The Boolean function $Y = AB + CD$ is to be realized using only 2-input NAND gates. The minimum number of gates required is _____.

Q.2 Which one of the following is the correct output (f) of the below circuit ?




- (A) $(a + b)(c + \bar{d})$ (B) $(\bar{a} + \bar{b})(c + \bar{d})$ (C) $(a + \bar{b})(c + \bar{d})$ (D) $(a + b)(\bar{a} + \bar{d})$

Q.3 The Boolean expression $Y(A, B, C) = A + BC$ is to be realized using 2-input gates of only one type. What is the minimum number of gates required for the realization ? _____.

Q.4 The minimum number of 2-input NAND gates required to implement the Boolean function $Z = A\bar{B}C$, assuming that A , B and C are available is [GATE 1998, IIT Delhi]

- (A) two (B) three (C) five (D) six

Q.5


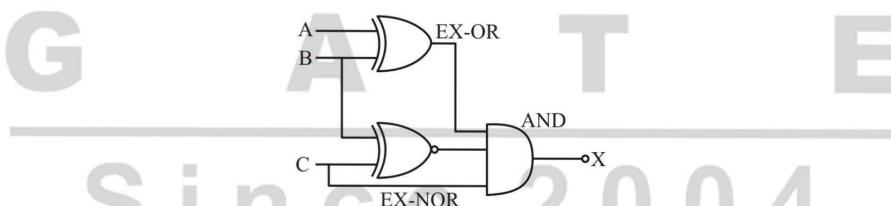


For the logic circuit shown in the above figure, what is the required input condition (A, B, C) to make output $X = 1$?

- (A) 1, 0, 1 (B) 0, 0, 1 (C) 1, 1, 1 (D) 0, 1, 1

Q.6 Match the logic gates in Column A with their equivalents in Column B. [GATE 2010, IIT Guwahati]

| Column A | Column B |
|----------|----------|
| P. | 1. |
| Q. | 2. |

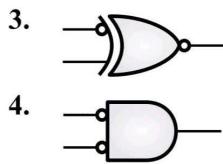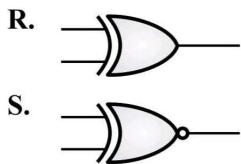

Codes : P Q R S

- (A) 2 4 1 3
 (B) 4 2 1 3
 (C) 2 4 3 1
 (D) 4 2 3 1


Q.7 Which one of the following expressions does NOT represent exclusive NOR of x and y?

[GATE 2013, IIT Bombay]

- (A) $xy + x'y'$ (B) $x \oplus y'$ (C) $x' \oplus y$ (D) $x' \oplus y'$

Q.8 For the output F to be 1 in the logic circuit shown, the input combination should be

[GATE 2010, IIT Guwahati]

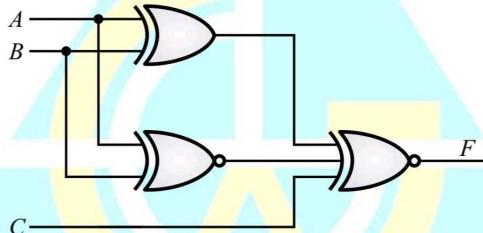

- (A) $A = 1, B = 1, C = 0$
 (B) $A = 1, B = 0, C = 0$
 (C) $A = 0, B = 1, C = 0$
 (D) $A = 0, B = 0, C = 1$

Q.9 Let $x_1 \oplus x_2 \oplus x_3 \oplus x_4 = 0$ where x_1, x_2, x_3, x_4 are Boolean variables, and \oplus is the XOR operator.

Which one of the following must always be TRUE?


[GATE 2016, IISc Bangalore]

- (A) $x_1 x_2 x_3 x_4 = 0$ (B) $x_1 x_3 + x_2 = 0$
 (C) $\bar{x}_1 \oplus \bar{x}_3 = \bar{x}_2 \oplus \bar{x}_4$ (D) $x_1 + x_2 + x_3 + x_4 = 0$

Q.10 Assume that only x and y logic input are available, and their complements \bar{x} and \bar{y} are not available. What is the minimum number of 2-input NAND gates required to implement $x \oplus y$? _____.

Q.11 All the logic gates shown in the figure have a propagation delay of 20 ns. Let $A = C = 0$ and $B = 1$ unit time $t = 0$. At $t = 0$, all the inputs flip (i.e. $A = C = 1$ and $B = 0$) and remain in that state. For $t > 0$, output Z = 1 for a duration (in ns) of _____.

[GATE 2015, IIT Kanpur]

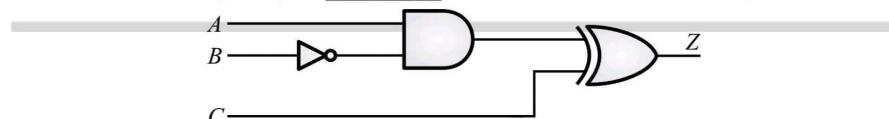

2. Boolean Algebra

Q.1 For the identity $AB + \bar{A}C + BC = AB + \bar{A}C$, the dual form is [GATE 1998, IIT Delhi]

- (A) $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$ (B) $(\bar{A}+\bar{B})(A+\bar{C})(\bar{B}+\bar{C}) = (\bar{A}+\bar{B})(A+\bar{C})$
 (C) $(A+B)(\bar{A}+C)(B+C) = (\bar{A}+\bar{B})(A+\bar{C})$ (D) $\bar{A}\bar{B} + A\bar{C} + \bar{B}\bar{C} = \bar{A}\bar{B} + A\bar{C}$


- Q.2** The Boolean function $x'y' + xy + x'y$ is equivalent to [GATE 2004, IIT Delhi]
- (A) $x' + y'$ (B) $x + y$ (C) $x + y'$ (D) $x' + y$
- Q.3** If x and y are Boolean variables which one of the following is the equivalent of $x \oplus y \oplus xy$ is
- (A) $x + \bar{y}$ (B) $x + y$ (C) 0 (D) 1
- Q.4** Let \oplus denote the exclusive OR(XOR) operation. Let '1' and '0' denote the binary constants. Consider the following Boolean expression for F over two variables P and Q

$$F(P, Q) = (1 \oplus P) \oplus (P \oplus Q) \oplus (P \oplus Q) \oplus (Q \oplus 0)$$

The equivalent expression for F is

- (A) $P + Q$ (B) $\overline{P+Q}$ (C) $P \oplus Q$ (D) $\overline{P \oplus Q}$


- Q.5** Consider the following circuit.

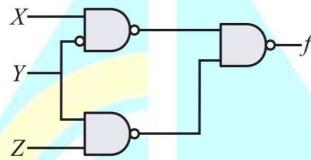

Which one of the following is TRUE?


- (A) f is independent of X (B) f is independent of Y
 (C) f is independent of Z (D) None of X, Y, Z is redundant

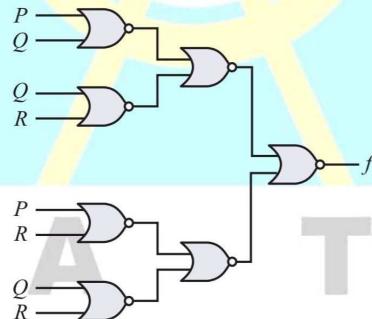- Q.6** What is the Boolean expression for the output f of the combinational logic circuit of NOR gates given below ? [GATE 2010, IIT Guwahati]



- (A) $\overline{Q+R}$ (B) $\overline{P+Q}$ (C) $\overline{P+R}$ (D) $\overline{P+Q+R}$

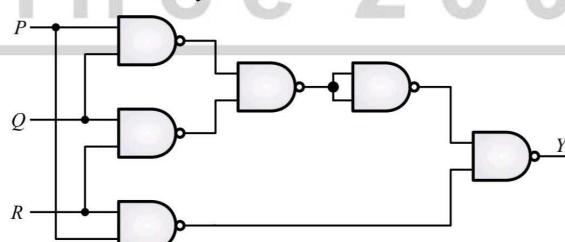- Q.7** The output Y in the circuit below is always "1" when [GATE 2011, IIT Madras]



- (A) two or more of the input P, Q, R are "0". (B) two or more of the inputs P, Q, R are "1".
 (C) any odd number of the inputs P, Q, R is "0". (D) any odd number of the inputs P, Q, R is "1".

Q.8 The Boolean expression $F(X, Y, Z) = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z} + XYZ$ converted into canonical product of sum (POS) form is [GATE 2015, IIT Kanpur]

- (A) $(X+Y+Z)(X+Y+\bar{Z})(X+\bar{Y}+\bar{Z})(\bar{X}+Y+\bar{Z})$
- (B) $(X+\bar{Y}+Z)(\bar{X}+Y+\bar{Z})(\bar{X}+\bar{Y}+Z)(\bar{X}+\bar{Y}+\bar{Z})$
- (C) $(X+Y+Z)(\bar{X}+Y+\bar{Z})(X+\bar{Y}+Z)(\bar{X}+\bar{Y}+\bar{Z})$
- (D) $(X+\bar{Y}+\bar{Z})(\bar{X}+Y+Z)(\bar{X}+\bar{Y}+Z)(X+Y+Z)$

Q.9 The product of sum expression of a Boolean function $F(A, B, C)$ of three variables is given by

$$F(A, B, C) = (A+B+\bar{C}).(A+\bar{B}+\bar{C}).(\bar{A}+B+C).(\bar{A}+\bar{B}+\bar{C})$$

The canonical sum of product expression of $F(A, B, C)$ is given by [GATE 2018, IIT Guwahati]

- (A) $\bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$
- (B) $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C}$
- (C) $A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$
- (D) $\bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + AB\bar{C}$

Q.10 The minterm expansion of $f(P, Q, R) = PQ + Q\bar{R} + P\bar{R}$ is [GATE 2010, IIT Guwahati]

- (A) $m_2 + m_4 + m_6 + m_7$
- (B) $m_0 + m_1 + m_3 + m_5$
- (C) $m_0 + m_1 + m_6 + m_7$
- (D) $m_2 + m_3 + m_4 + m_5$

Q.11 The simplified SOP (Sum of Product) form of the Boolean expression

$$(P + \bar{Q} + \bar{R}).(P + \bar{Q} + R).(P + Q + \bar{R})$$

is _____.

[GATE 2011, IIT Madras]

- (A) $(\bar{P}.Q + \bar{R})$
- (B) $(P + \bar{Q}.R)$
- (C) $(\bar{P}.Q + R)$
- (D) $(P.Q + R)$


Q.12 For the Boolean expression $f = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + abc + ab\bar{c}$ the minimized Product of sum (POS) expression is [GATE 2011, IIT Madras]

- (A) $f = (b+c).(a+c)$
- (B) $f = (\bar{b}+c).(\bar{a}+c)$
- (C) $f = (\bar{b}+c).(a+\bar{c})$
- (D) $f = \bar{c} + abc$

Q.13 The Boolean expression $X(P, Q, R) = \pi(0, 5)$ is to be realized using only two 2-input gates. Which are these gates?

- (A) AND and OR
- (B) NAND and OR
- (C) AND and XOR
- (D) OR and XOR

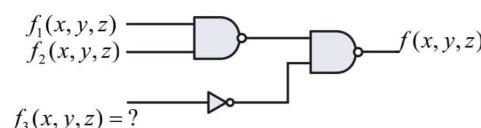Q.14 Consider the following logic circuit whose inputs are function f_1, f_2, f_3 and output is f .



Given that $f_1(x, y, z) = \Sigma(0, 1, 3, 5)$, $f_2(x, y, z) = \Sigma(6, 7)$ and $f(x, y, z) = \Sigma(1, 4, 5)$, f_3 is

[GATE 2002, IISc Bangalore]

- (A) $\Sigma(1, 4, 5)$
- (B) $\Sigma(6, 7)$
- (C) $\Sigma(0, 1, 3, 5)$
- (D) None of the above

Digital


Logic Gates

(1)

$$Y = AB + CD$$

→ 3 NAND Gate Size (p) Ans

(2)

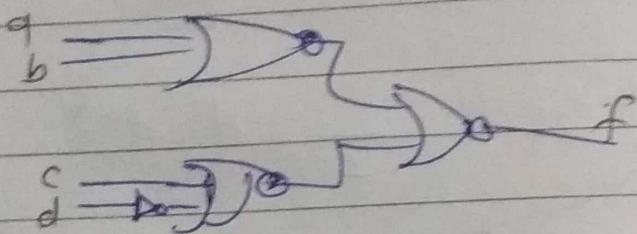

(A)

$$f = (a+b)(c+d)$$

Ans

(3)

$$Y = A + BC$$

$$Y = \overline{A}A + BC$$


→ 3 NAND Gate

Ans

(4)


$$Z = A\bar{B}C$$

$$= (\bar{A}C) \cdot \bar{B}$$


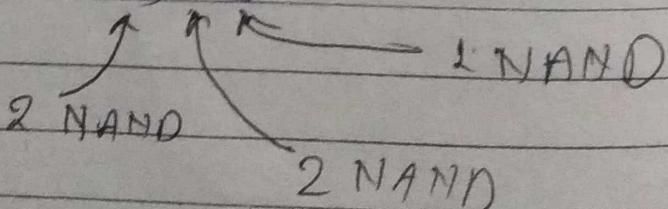


$$\text{Total} = 5$$

Ans

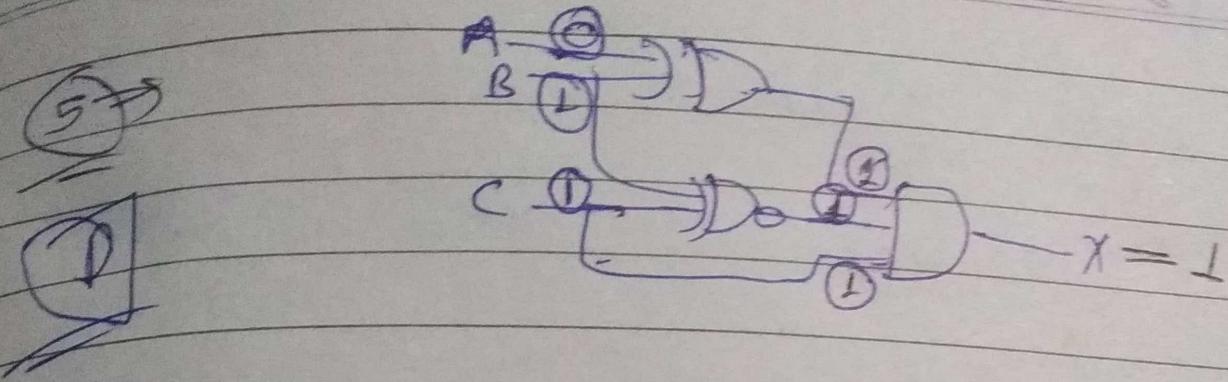


$(A, B, C) \in \{0, 1\}^3$ Ans

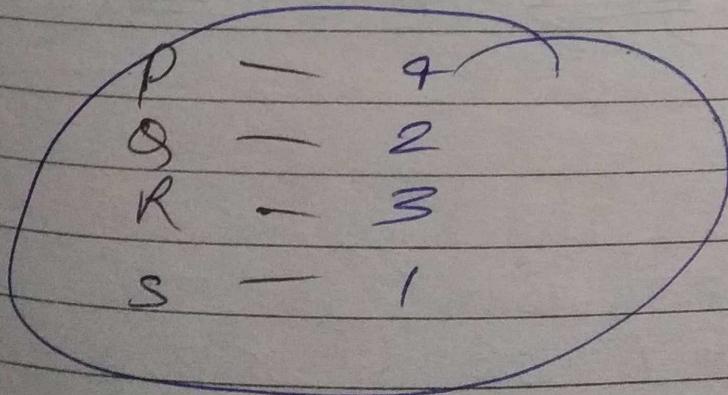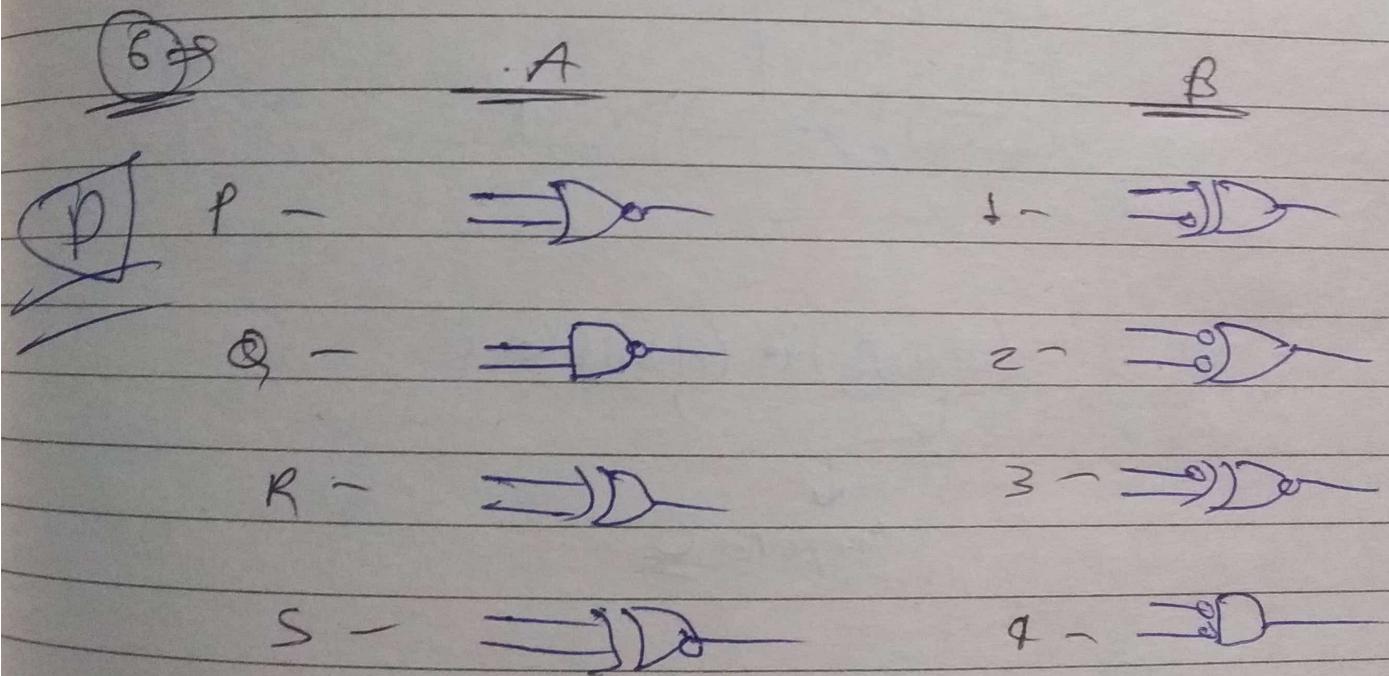

⑦ →

Nat XNOR -

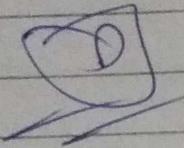


$$x' \oplus y' = \overline{x \oplus y} = \overline{x \oplus y}$$

→ XOR

⑧ →

A, B, C

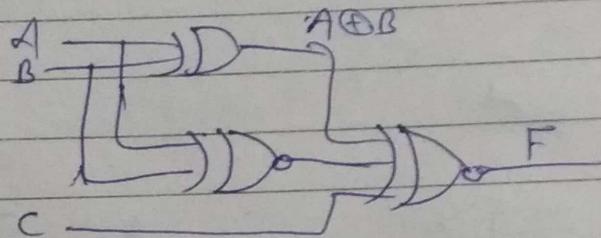

$$F = (A \oplus B) \odot (A \odot B) \odot C$$

↓
Simplify = 0

$$F = 0 \odot C$$

F = \bar{C} $\Rightarrow \bar{C} = 1 \Rightarrow C = 0$

A
B
C

$$= A = 1, B = 1, C = 0$$

$$= A = 1, B = 0, C = 0$$

$$= A = 0, B = 1, C = 0$$

(3) $x_1 \oplus x_2 \oplus x_3 \oplus x_4 = 0$


(c) $x_1 \oplus x_3 = x_2 \oplus x_4$

$\underline{x_1 \oplus x_3} = \underline{x_2 \oplus x_4}$

$x_1 \oplus \bar{x}_3 = \bar{x}_2 \oplus \bar{x}_4$ } Ans

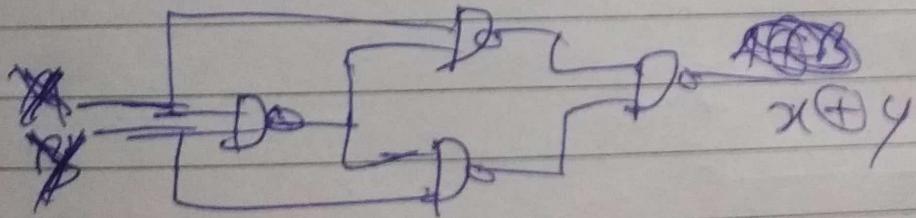
(4)

Minimum 2-Input NAND $\rightarrow (x \oplus y)$




Minimum = 9 } Ans

(1) \rightarrow

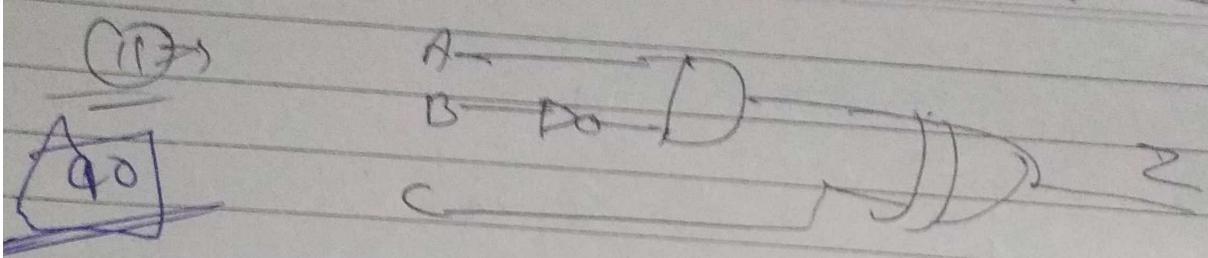

$$A = C = 1, \quad B = 0$$

$t=0$

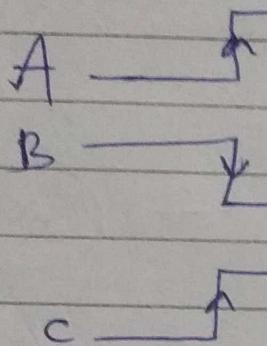

(0ns) $\overline{B} = \uparrow$

$t=20$

(20ns) $\overline{B} = \uparrow$

20

(0ns) $A\overline{B} = \uparrow$

$t=40ns$

(40ns) $A\overline{B}$

0

40

(0ns)

$A\overline{B} \oplus C$

20

60

(20ns)

$A\overline{B} \oplus C$

\leftarrow 40ns \rightarrow One

Boolean
Algebra

1) $AB + \bar{A}C + BC = AB + \bar{A}C$

2) Apply dual

$$(A+B) \cdot (\bar{A}+C) \cdot (B+C) = (A+B)(\bar{A}+C)$$

3) $\bar{x}\bar{y} + xy + \bar{x}y$

4) $\bar{x}\bar{y} + (\bar{x}y) + xy + (\bar{x}y)$
 $\bar{x}(\bar{y}+y) + \bar{y}(x+\bar{x})$
= $\bar{x} + y$ Ans

5) $x \oplus y \oplus xy$

6) $(x \oplus y)x\bar{y} + (x \oplus y)\bar{x}\bar{y}$
 $(x\bar{y} + \bar{x}\bar{y})x\bar{y} + (\bar{x}\bar{y} + x\bar{y})\bar{x} + \bar{y}$

$xy + \bar{x}\bar{y} + x\bar{y}$

$x + y$ Ans


Q

$$(1 \oplus P) \oplus (P \oplus Q) \oplus (P \oplus Q) \oplus (Q \oplus 0)$$

P

$$\begin{aligned} & \overline{P} \oplus 0 \oplus Q \\ & \overline{P} \oplus Q \\ & = \overline{P \oplus Q} \end{aligned}$$

5

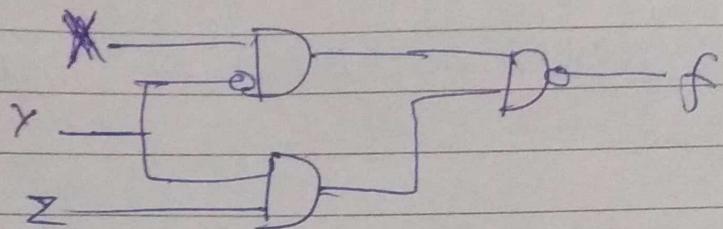

P

$$f = \overline{x}\overline{y} + \overline{y}z$$

Independent, x, y, z

6

$$Q + PR + P + PQ$$

$Q + R$ Ans

A

7

$$Y = PQ + QR + PR$$

B

Two or more of the i/p
P, Q, R are '1'

(8)


$$F = \bar{x}yz + xy\bar{z} + xy\bar{z} + xyz$$

(A)

$$= \sum m(010, 100, 110, 111) \\ = \sum m(2, 4, 6, 7)$$

$$= \pi M(1, 3, 5, 7)$$

$$= \pi M(000, 001, 011, 101)$$

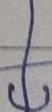

$$F = (x+y+z)(x+y+\bar{z})(x+\bar{y}+\bar{z})(\bar{x}+y+\bar{z})$$

Ans

(9)

$$F = (A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+B+C)(\bar{A}+\bar{B}+C)$$

(B)

$$= \pi M(001, 011, 100, 111)$$

$$= \pi M(1, 3, 4, 7)$$

$$= \sum m(0, 2, 5, 6)$$

$$= \sum m(000, 010, 101, 110)$$

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + AB\bar{C}$$

Ans

(10)

$$f = PQ + QR + PR$$

A

$$11X \times 10 \quad 1X9$$

$$\begin{array}{r} 110 \\ 111 \end{array} \quad \begin{array}{r} 010 \\ 110 \end{array} \quad \begin{array}{r} 100 \\ 110 \end{array}$$

$$6 \otimes 7 \quad 2 \otimes 6 \quad 9 \otimes 3$$

2, 8, 6, 7

$$m_2 + m_4 + m_6 + m_7$$

Ans

(11)

$$(P + \bar{Q} + \bar{R})(P + \bar{Q} + R)(P + Q + \bar{R})$$

B

$$= (P + \bar{Q} + \bar{R} \cdot R) (P + Q + \bar{R})$$

$$= (P + \bar{Q}) (P + Q + \bar{R})$$

$$= P + \bar{Q} (Q + \bar{R})$$

$$P + \bar{Q} \bar{R}$$

Ans

12)

$$\begin{aligned}
 f &= \bar{a}\bar{b}\bar{c} + \bar{a}bc + \cancel{\bar{a}b\bar{c}} + abc + ab\bar{c} + a\bar{b}\bar{c} \\
 &= \bar{c}(\bar{a}\bar{b} + \bar{a}b + ab + a\bar{b}) + abc \\
 &= \bar{c} \cdot 1 + abc \\
 &= (\bar{c} + a)(\bar{c} + b)(\bar{c} + c) \\
 &= (a + \bar{c})(b + \bar{c})
 \end{aligned}$$

Ans

13)

$$X = \pi(0, 5)$$

TP

$$=\pi M(000, 101)$$

$$= (P + Q + R)(\bar{P} + Q + \bar{R})$$

$$= Q + (P + R)(\bar{P} + \bar{R})$$

$$= Q + (PR + R\bar{P})$$

$$= Q + (P \oplus R)$$

XOR XOR

14)

$$\begin{array}{l}
 f_1 \xrightarrow{0, 1, 3, 5} 0, 1, 2, 3, 4, 5, 6, 7 \\
 f_2 \xrightarrow{6, 7} \\
 f = 1, 4, 5
 \end{array}$$

TP

$$\begin{array}{l}
 f_3 \xrightarrow{} 0, 1, 2, 3, 6, 7 \\
 f = 1, 4, 5
 \end{array}$$

ANS